

## Board4 report: Instrument Droid

### Objective


To design a board that is capable of measuring Rthevenin of any voltage supply up to 12V automatically based on the Atmega328 microcontroller.

### Plan of Record (POR)

The circuit should have,

1. A power plug for “AC to 5V DC adaptor” to supply power for the board.
2. A power plug for” measuring Rthevenin wall wart”, a connector to plug in the power supply using jumpers, and a USB C connector.
3. An OLED display for showing the Rthevenin.
4. Additionally, 3 smart LEDs and a buzzer as aesthetic features.
5. A USB mini-B with TVS diode for connecting to PC.
6. A MOSFET, Op-Amp, ADC, and DAC
7. A switch to select between 5V/USB supply.
8. ICSP header pin for bootloading Atmega 328.
9. Atmega 328 microcontroller and CH340g for USB to UART.
10. 0.5Ω sense resistor and a test point to measure inrush current
11. A reset circuitry
12. A ferrite filter on AVCC pin.
13. Crystal:16MHz for Atmega328 and 12MHz for CH340g
14. Indicator LED for the power supply and VRM
15. Test points for 5V rail, I2C, UART, USB (D+, D-)
16. Isolation header pins for Atmega 328
17. A switch for selecting Rsense 1/10 ohm at the source of the MOSFET

### Napkin Sketch:

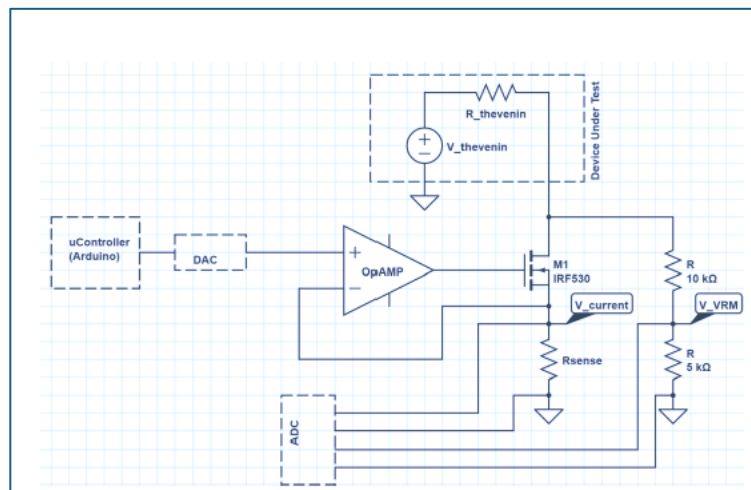


## Components Required/ BOM:


Comment	Description (Short)	Designator	Footprint	LibRef	Qty
AT-1224-TWT-5V	5V buzzer	BZ1	BUZZER-TH	BUZZER_1	1
22uF	Capacitor 22µF 1206	C1, C7-C10, C12-C20	1206_Passive_Capacitor	C_22uF_1206	13
22pF	Capacitor 22pF 1206	C3-C6	1206_Passive_Capacitor	C_22pF_1206	4
1uF	Capacitor 1µF 1206	C11, C14	1206_Passive_Capacitor	C_1uF_1206	2
IN-PI55Q	RGB LED SMD	D1-D3	SERIAL_LED	LED_Smart	3
NRPN032PA EN-RC	ICSP header 6-pin	J1	ICSP	J_ICSP	1
USB Mini	USB Mini-B	J2	USB_MINI_B	J_USB_B_Mini	1
FB_10uH_1206	Inductor 10µH 1206	L1	AIML-1206	FB_10uH_1206	1
Red LED	LED Red 1206	LED1, LED3-LED6	LED_1206	LED_RED_1206	5
Power Jack	Barrel jack	P1, P2	Power Jack	P_Power_Jack	2
2P Terminal Block	Terminal block	P3	TerminalBlock_3.5mm	P_TerminalBlock	1
500mΩ	Resistor 500mΩ	R1	1206_Passive_Resistor	R_500mOhm_1206	1
1MΩ	Resistor 1MΩ	R2, R3	1206_Passive_Resistor	R_1M_1206	2
1kΩ	Resistor 1kΩ	R4, R6-R8, R10	1206_Passive_Resistor	R_1K_1206	5
10kΩ	Resistor 10kΩ	R9, R11, R14, R15, R18, R19	1206_Passive_Resistor	R_10K_1206	6
10Ω	Resistor 10Ω	R12	1206_Passive_Resistor	R_10Ohm_1206	1
1Ω	Resistor 1Ω	R13	1206_Passive_Resistor	R_1Ohm_1206	1
0Ω	Jumper resistor	—	1206_Passive_Resistor	R_0Ohm_1206	2
PREC003SAA N	3-pin switch header	SW1, SW4, SW5	3_PIN_100mil	SW_3Pin_100mil_Switch	3
2-pin switch header	2-pin header	SW2	2Pin_Header	SW_2Pin_100mil_Switch	1

TL3305AF16 0QG	Tactile switch SMD	SW3	Switch_JLC	SW_Push_Button_J LC	1
10x Probe TP	Test points	TP1, TP3, TP3/+5V, TP4-TP8, TP-D-, TP- D+	TP10x_Probe	TP_10x_Probe	10
ATMEGA328 P-ANR	Microcontr oller	U1	ATMega328P	U_ATMega328P	1
CH340G	USB-serial IC	U2	USB_to_serial	U_USBtoSerial	1
MCP6002T- I/SN	Dual op- amp	U3	SOIC-8	U_MCP6002T-I/SN	1
ADS1115DG SR	16-bit ADC	U4	VSSOP-10	U_ADC_ADS1115I DGSR	1
MCP4725	12-bit DAC	U5	SOT23-6	U_MCP4725A0T- E/CH	1
AO3400A	N-MOSFET	Qx	N-MOSFET	Q_Nch_MOSFET	1
X322512MS B4SI	12 MHz crystal	Y1	SMD-3225	X_12MHz_Res	1
X322516MLB 4SI	16 MHz crystal	Y2	SMD-3225	X_16MHz_Res	1


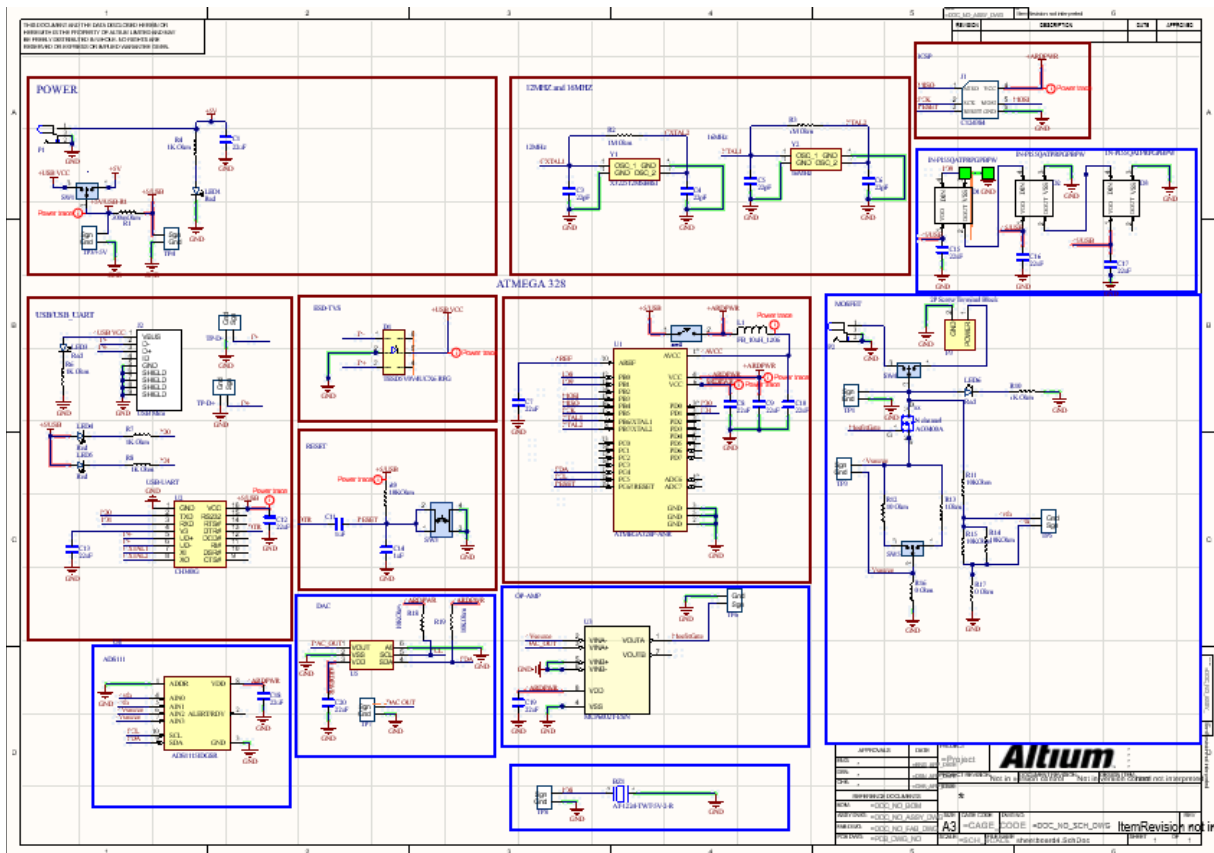
**Schematic: Instrument Droid Schematic in Altium software**



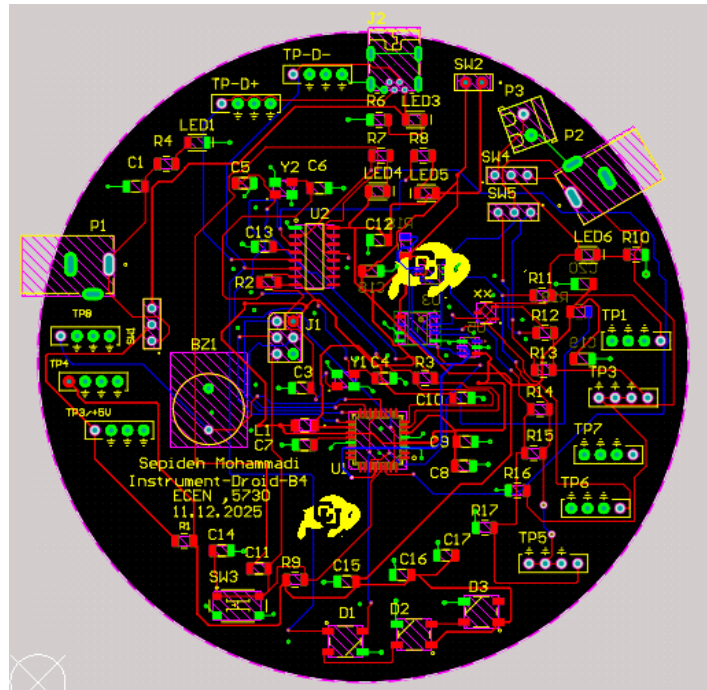
**Layout: Instrument layout done in Altium Software**





**3D View: front view and back view**

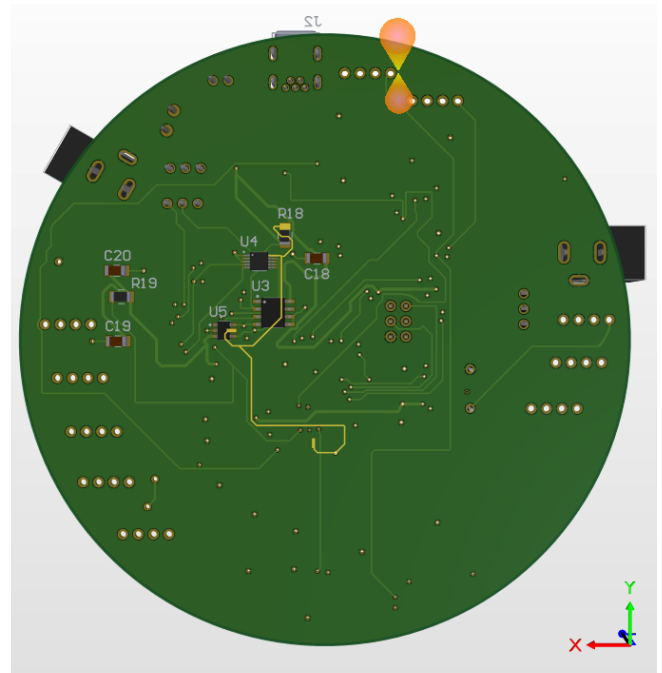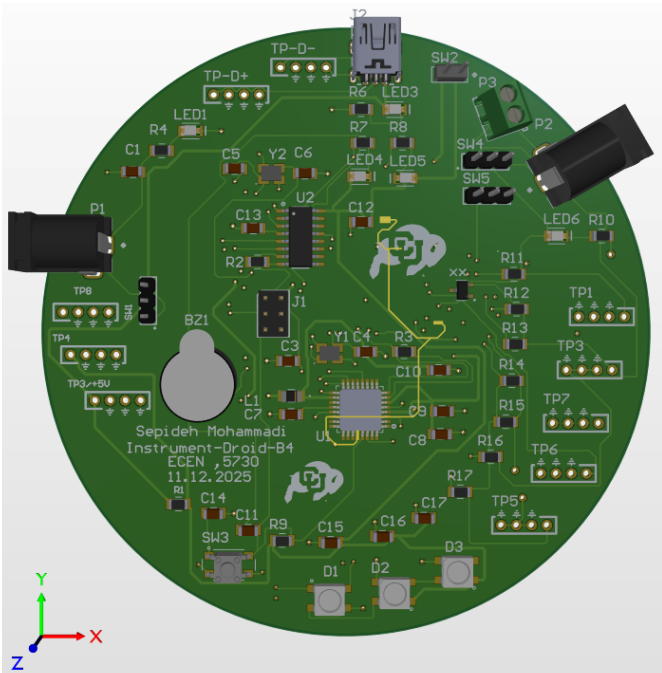

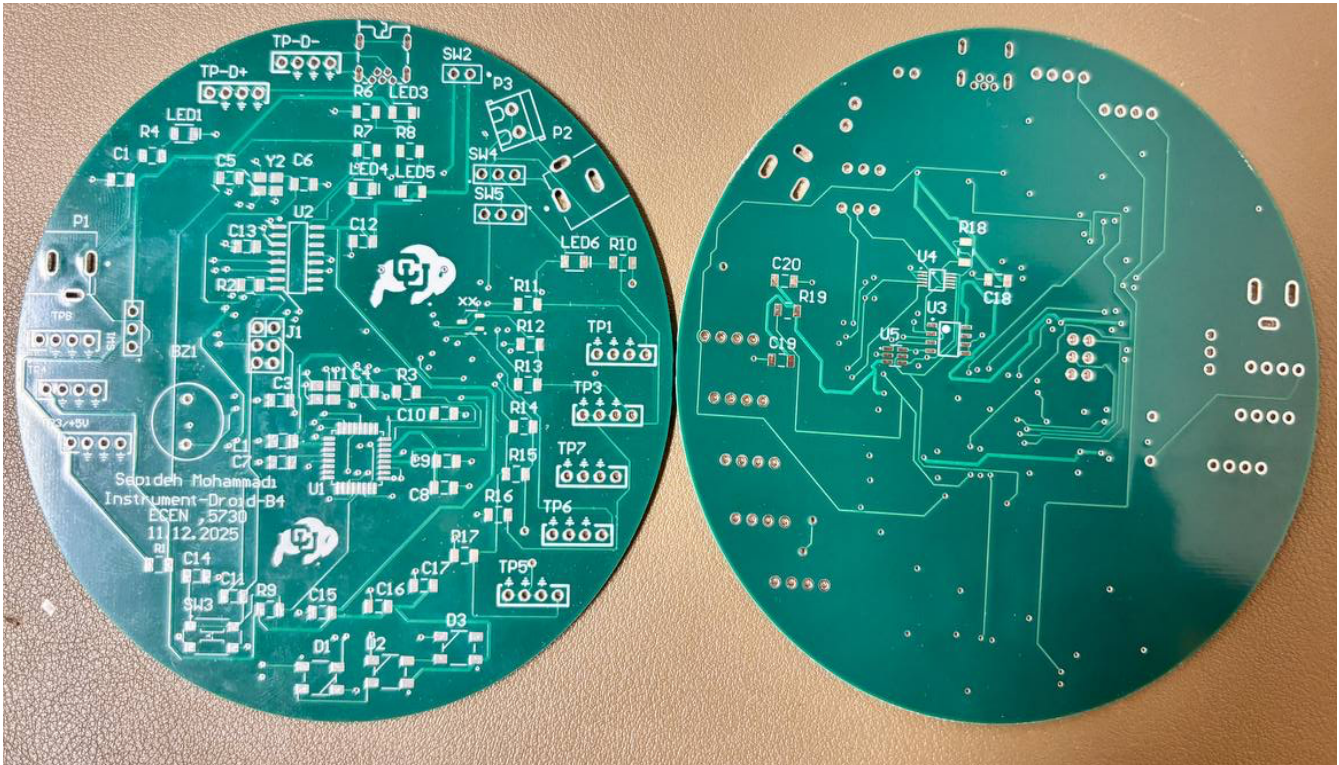**Before assembling: Unassembled from front / Unassembled board-back**



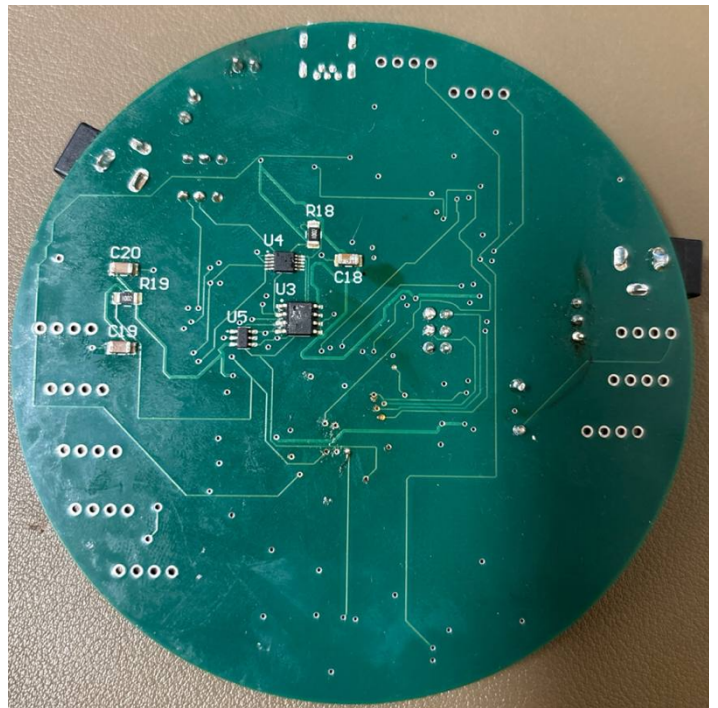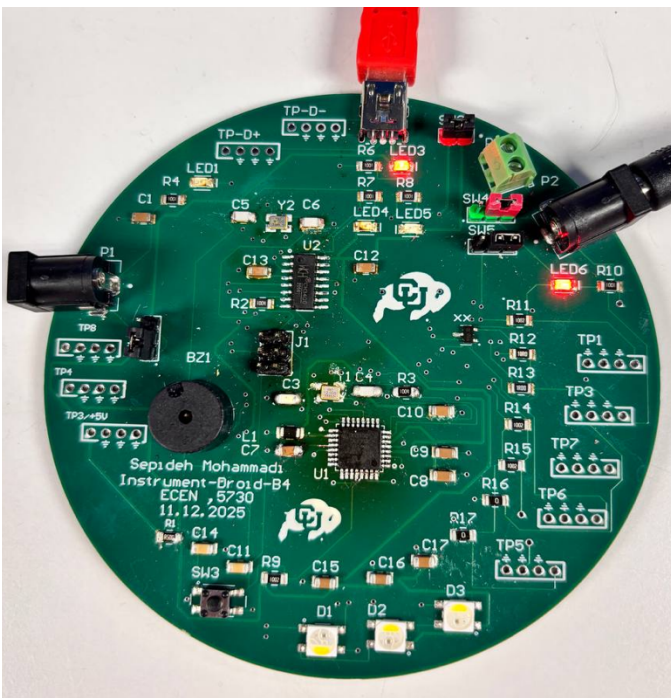
**After assembling: Assembled board-front / Assembled board-back**




## What it means to work

1. Indicator LED1 should turn ON and if VRM is connected, LED4 should be ON.
2. The board can be powered with a 5 V AC to DC adapter /USB which can be measured at TP3/+5V
3. Using a commercial Arduino UNO programmed as ISP, the Atmega can be boot loaded to turn it into Arduino UNO using ICSP/ SPI header pins
4. After bootloading, 16MHz crystal should resonate at 16MHz and it should run codes uploaded from IDE.
5. It should be able to measure Rthevenin of any power supply up to 12V after uploading the appropriate code.

## Bootloader procedure:

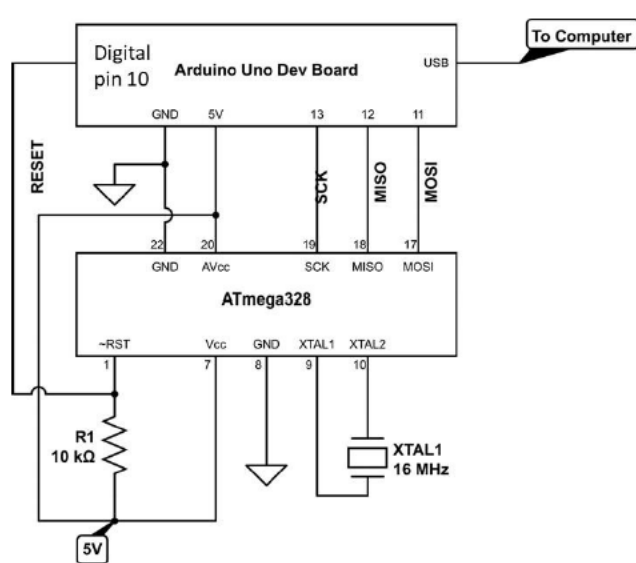

- Connect SCK of ICSP to D13 of UNO
- MISO of ICSP to D12 of UNO
- MOSI of ICSP to D11 of UNO
- VCC and gnd of ICSP to 5V header and gnd socket of UNO
- Reset header pin of ICSP to D10 of UNO
- After this is done, connect commercial Arduino to PC and go to
- File>examples>11(Arduino ISP), upload it.
- Tools>programmer (Arduino as ISP) and make sure port and board is selected appropriately. Then click Burn bootloader.

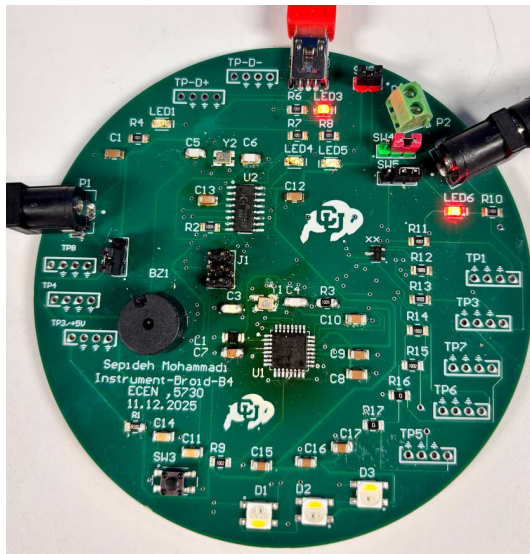

## What worked/ Bring-up:

All the anticipated LEDs turned ON, the ATMEGA 328 is boot-loaded successfully using ICSP. After uploading the appropriate code, it was able to measure Rthevenin.

## What did not work?

Everything worked as expected and there were no Hard/soft errors.

## Scope shots and Analysis

- Figure 1 indicates 5V (Yellow) and 5V -5VVRM (Green) measured at TP3/+5V and TP5 respectively. Figure 2 shows DAC signal when the code is running.

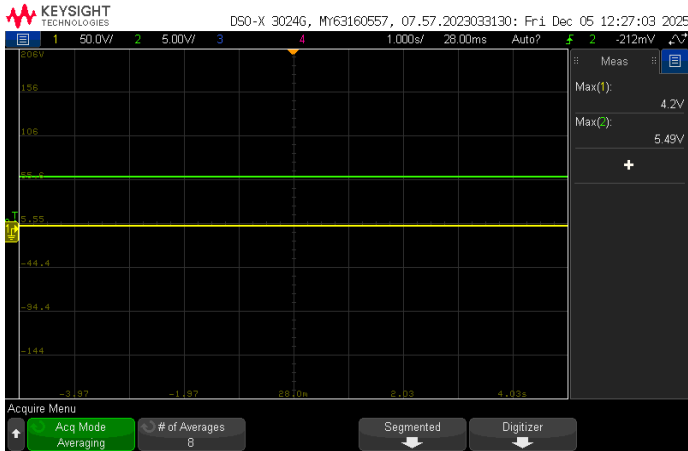


Figure 1 Power Rails (5V and 5- VRM).

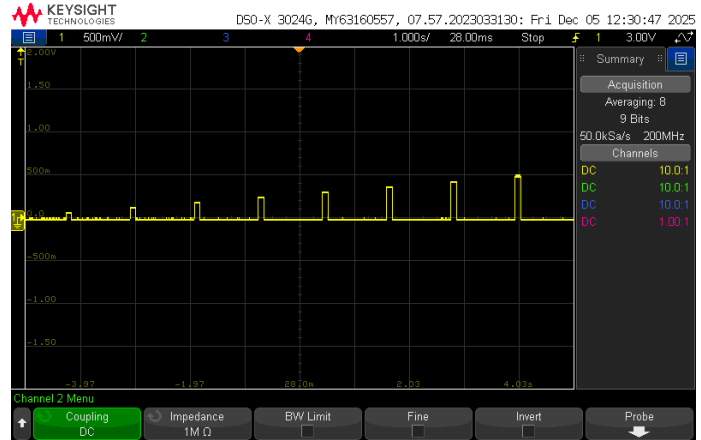


Figure 2 DAC signal

- USB signals are sniffed from TP-D+, and TP-D-respectively when the code is uploaded. It is captured using Normal trigger mode. I2C and RESET signals: I2C and RESET signals are sniffed from TP6 and directly from the bottom for the reset and ICSP respectively. It is captured using Normal trigger mode.

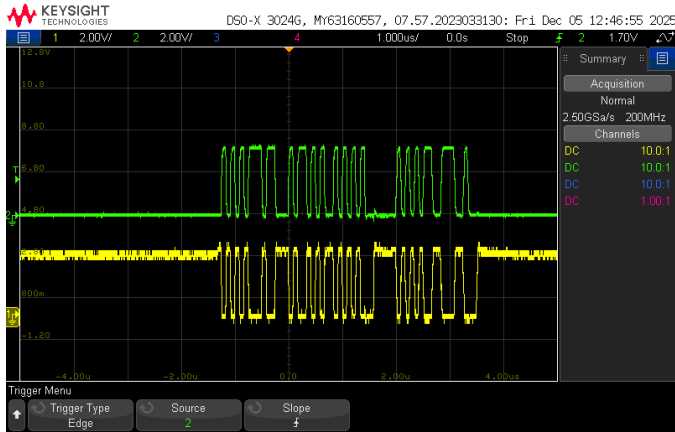


Figure 3 USB signals, yellow – D-, Green- D+



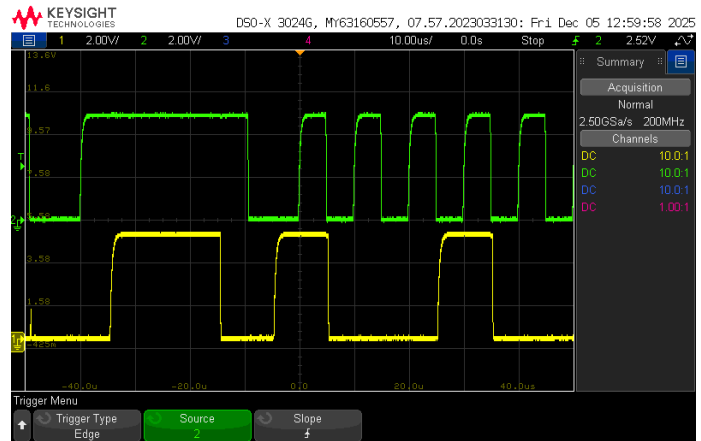


Figure 4 I2C signal, yellow - SCL, green-SDA

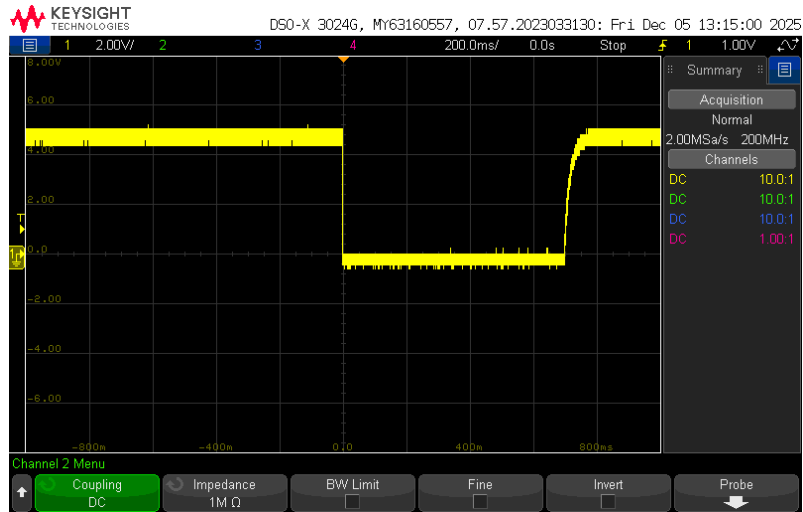


**Figure 5: RESET signal when switch is pressed. I measured it directly from the push bottom.**

**3. Inrush current:** With normal trigger mode, the inrush current sunk by the decoupling capacitors is captured across 0.5Ω. In Figure 19, Yellow is the high side of the resistor, green is the low side, and pink is the math function that subtracts the high side from the low side. So, Inrush current =  $2.57/0.5 = 5.14\text{A}$ !

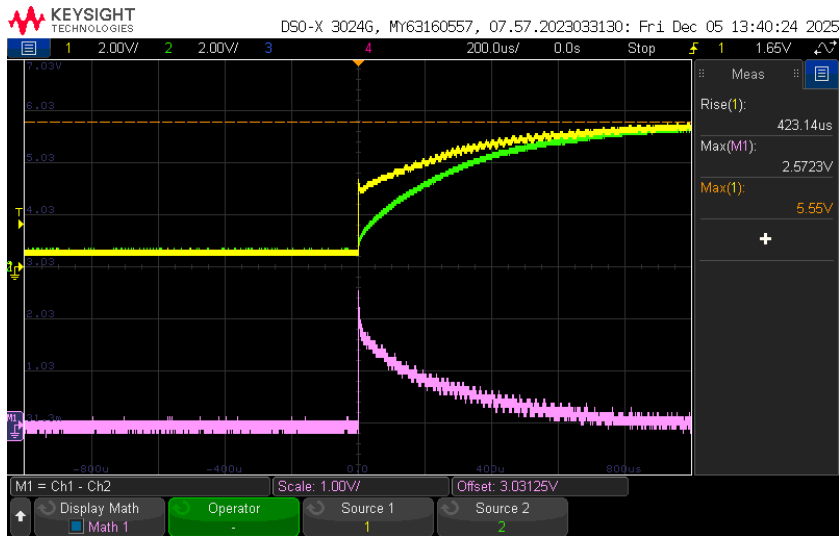

**Figure 6: Inrush Current**

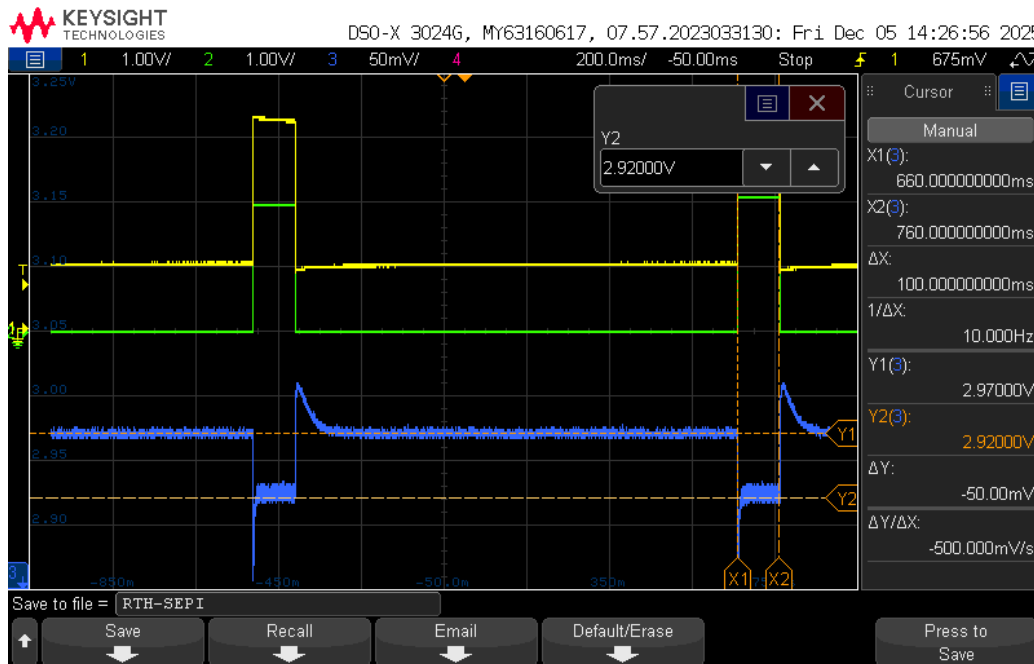1. GATE, Vth, Vload signals for Thevenin Resistance: This is an instance where Gate signal, Vth and Vload are captured at test points, when a **5v wall wart is connected to VRM**.



## Rth Calculation (Using New Scope Data)

We calculate the source output resistance using:

$$R_{th} = \frac{V_{th} - V_{load}}{I_{load}}$$

### 1. Read voltages from the oscilloscope

From the new image:

- **Before dip (blue trace):**

$$V_{meas,before} = 2.97 \text{ V}$$

- **During dip (blue trace):**

$$V_{meas,dip} = 2.92 \text{ V}$$

### 2. Convert measured voltage to actual voltage

The blue signal is measured **after a voltage divider**:  
10 k $\Omega$  (top) and 5 k $\Omega$  (bottom)

Divider ratio:

$$\frac{5k}{10k + 5k} = \frac{1}{3}$$

So, the real voltage is:

$$V_{\text{actual}} = 3 \times V_{\text{measured}}$$

**Actual Vth (before dip)**

$$V_{th} = 2.97 \times 3 = 8.91 \text{ V}$$

**Actual Vload (during dip)**

$$V_{load} = 2.92 \times 3 = 8.76 \text{ V}$$

### 3. Load current calculation

Green trace shows **1.5 V across a 10  $\Omega$  resistor**:

$$I_{load} = \frac{1.5}{10} = 0.15 \text{ A}$$

So, the load current is:

$$I_{load} = 150 \text{ mA}$$

### 4. Compute Rth

$$R_{th} = \frac{V_{th} - V_{load}}{I_{load}}$$


$$R_{th} = \frac{8.91 - 8.76}{0.15}$$

$$R_{th} = \frac{0.15}{0.15} = 1\Omega$$

The following values are copied from serial monitor of Arduino IDE to Excel for analysis. The graphs show the non-linear behavior of power supplies.


With 5V wall wart: 0.2 ohms

Index	Iload (mA)	Vth (V)	Vload (V)	Rthev ( $\Omega$ )
1	12.387	5.3529	5.3492	0.3002
2	25.066	5.3532	5.3476	0.2251
3	37.853	5.3525	5.3391	0.3521
4	50.566	5.3530	5.3297	0.4602
5	63.537	5.3526	5.3208	0.5091
6	76.250	5.3527	5.3137	0.5108
7	89.903	5.3524	5.3043	0.5431
8	101.543	5.3524	5.2957	0.5588
9	114.199	5.3527	5.2604	0.8082
10	127.073	5.3528	5.2493	0.8144
11	139.812	5.3530	5.2362	0.8354
12	152.398	5.3526	5.2238	0.8450
13	165.057	5.3521	5.2089	0.8467
14	178.050	5.3527	5.2017	0.8482
15	191.024	5.3521	5.1898	0.8588
16	203.908	5.3526	5.1789	0.8522
17	216.738	5.3529	5.1664	0.8603
18	229.426	5.3529	5.1570	0.8540
19	242.243	5.3524	5.1461	0.8518
20	255.091	5.3528	5.1352	0.8530

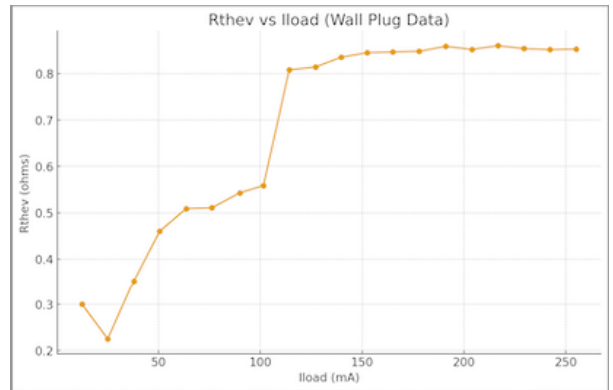


### With 3.3V Arduino Data Table

Index	Iload (mA)	Vth (V)	Vload (V)	Rthev ( $\Omega$ )
1	12.389	3.3593	3.3562	0.2530
2	25.070	3.3593	3.3532	0.2450
3	37.850	3.3593	3.3500	0.2454
4	50.563	3.3593	3.3470	0.2420
5	63.537	3.3593	3.3438	0.2434
6	76.250	3.3593	3.3407	0.2441
7	88.882	3.3593	3.3374	0.2460
8	101.529	3.3592	3.3217	0.3699
9	114.185	3.3593	3.2874	0.6296
10	127.055	3.3593	3.2522	0.8431
11	139.800	3.3593	3.2178	1.0127
12	152.390	3.3593	3.1841	1.1493
13	165.045	3.3593	3.1472	1.2790
14	178.038	3.3594	3.1148	1.3740
15	191.014	3.3593	3.0800	1.4633
16	203.912	3.3594	3.0461	1.5367
17	216.745	3.3594	3.0116	1.6045
18	229.424	3.3594	2.9778	1.6633
19	242.225	3.3594	2.9438	1.7159
20	255.080	3.3595	2.9091	1.7658

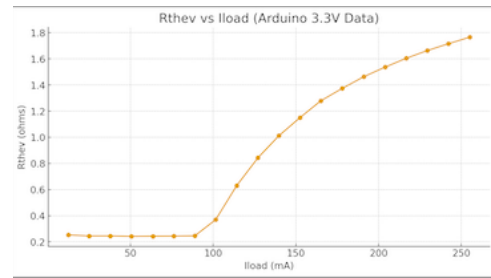

**Function Generator Table: With Function generator using jumper (@P2 ref designator): 50 ohms**

Index	Iload (mA)	Vth (V)	Vload (V)	Rthev ( $\Omega$ )
1	12.396	9.6039	9.0085	48.0272
2	25.089	9.6040	8.3990	48.0293
3	37.880	9.6040	7.7847	48.0285
20	50.615	9.6039	7.1727	48.0343

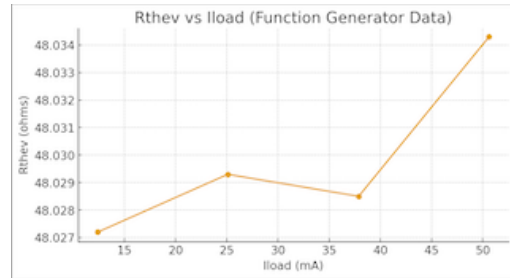

**Best design practices followed:**

1. During component selection, unique parts were reduced.
2. The decoupling capacitor is placed near the ICs, and a ferrite bead is used for the AVCC pin which is more sensitive to noises.
3. 3 X 3 inches board dimensions are used which has the lower cost at JLC PCB fabrication vendor
4. Test points were labeled to reduce soft errors.
5. Indicator LED and isolation switches were included for faster debugging/ troubleshooting.
6. Continuous return planes are used in layer 2 and layer 3.
7. Signal transitions between layers were surrounded by stitching ground vias for signal integrity.
8. 20 mil width is used for power traces (ensures high current carrying capacity) and 6 mil width for all other traces (ensures highest routing density with lowest cost allowed by the fabrication vendor).

**Things could be improved.**

1. The board can be made smaller by making a custom footprint for test points
2. OLED has pins in the following order: VCC, Gnd, SCL, SDA. But most of the stock available online is of the order: Gnd, VCC, SCL, SDA. So, this order should be followed for the next implementation of OLED.

**Conclusion**

The designed instrument droid is successfully able to measure Rthevenin of the power supplies which is rare data to be found in the datasheet. This is important as it characterizes the first-order model of the power supply.

```

1 // vrm characterizer board
2 #include <Wire.h>
3 #include <Adafruit_MCP4725.h>
4 #include <Adafruit_ADS1X15.h>
5 Adafruit_MCP4725 dac;
6 // OLED
7 #include <Adafruit_GFX.h>
8 #include <Adafruit_SSD1306.h>
9 // #include <Fonts/FreeSerif9pt7b.h>
10 #define SCREEN_WIDTH 128
11 #define SCREEN_HEIGHT 64
12 Adafruit_SSD1306 display(SCREEN_WIDTH, SCREEN_HEIGHT, &Wire, -1);
13 // LED
14 #include <Adafruit_NeoPixel.h>
15 #ifdef __AVR__
16 #include <avr/power.h>
17 #endif
18
19 #define LEDPIN 9
20 Adafruit_NeoPixel pixels(3, LEDPIN, NEO_GRB + NEO_KHZ800);
21 // buzzer
22 float R_sense = 10.0; // current sense resistor
23 long itime_on_msec = 100; // time for taking measurements
24 long itime_off_msec = 10; // time to cool off
25 int icounter_off = 0; // counter for number of samples off
26 int icounter_on = 0; // counter for number of samples on
27 float V_divider = 5000.0 / 15000.0; // voltage division on VRM measurement
28 int t_step_iA = 1; // ramp step of DAC
29 int I_A = 0; // current in A (ADU to A conversion)
30 float V_RM_on_v, V_RM_off_v;
31 float I_sense_on_A, I_sense_off_A;
32 float R_thevenin;
33 int npts = 20; // number of measurement steps
34 // values for converting ADC readings
35 float ADC_V_per_ADU = 1.0 / 1875.0; // ADS1115 in GAIN_TWOTHIRDS
36 float ADC_V_per_ADU_2 = 1.0 / 1875.0;

```

```

37 // SETUP
38 //-----
39 void setup() {
40   Serial.begin(115200);
41   pinMode(8, OUTPUT); // buzzer
42   pixels.begin();
43   if (!display.begin(SSD1306_SWITCHCAPVCC, 0x3C)) {
44     Serial.println("SSD1306 allocation failed");
45     for(;;);
46   }
47   display.clearDisplay();
48   display.setTextSize(2);
49   display.setTextColor(WHITE);
50   display.setCursor(1, 0);
51   display.println("Instrument");
52   display.setCursor(0, 40);
53   display.println("Measures Rthev");
54   display.display();
55   delay(1000);
56   display.clearDisplay();
57   display.display();
58   dac.begin(0x60); // MCP4725 default address
59   dac.setVoltage(0, false); // start at 0 output
60   Adafruit_ADS1115 ads;
61   ads.setGain(GAIN_TWOTHIRDS); // gain setting
62   ads.begin();
63   ads.setDataRate(RATE_ADS1115_860SPS);
64 // MAIN LOOP
65 //-----
66 void loop() {
67   pixels.clear();
68   pixels.show();
69   noTone(8);
70   for (int i = 1; i <= npts; i++) {
71     display.clearDisplay();
72     I_A = i * t_step_iA;
73     dac.setVoltage(I_A, false); // output current step
74     // MEASURE WITH LOAD ON
75     func_meas_on();
76     // MEASURE WITH LOAD OFF

```

```

89   Serial.print(" ");
90   Serial.print(V_RM_loaded_v, 4);
91   Serial.print(" ");
92   Serial.println(R_thevenin, 4);
93 //-----
94 // OLED Output
95 //-----
96 display.setCursor(0, 0);
97 display.setTextSize(1);
98 display.print("index: ");
99 display.print(i);
100 display.display();
101 display.setCursor(0, 10);
102 display.print("I=");
103 display.print(I_load_A * 1000.0, 1);
104 display.print(" mA");
105 display.display();
106 display.setCursor(0, 20);
107 display.print("Vth=");
108 display.print(V_RM_thevenin_v, 4);
109 display.print(" V");
110 display.display();
111 display.setCursor(0, 30);
112 display.print("Vload=");
113 display.print(V_RM_loaded_v, 4);
114 display.print(" V");
115 display.display();
116 display.setCursor(0, 40);
117 display.print("Rth=");
118 display.print(R_thevenin, 3);
119 display.print(" ohms");
120 display.display();
121 tone(8, 1000, 50);
122 pixels.clear();
123 pixels.setPixelColor((i % 3), pixels.Color(255, 50, 0));
124 pixels.show();
125 }

```

```

Serial.println("done!");
}
//-----
// MEASUREMENT FUNCTIONS
//-----
void func_meas_off() {
  dac.setVoltage(0, false); // remove load
  icounter_off = 0;
  V_RM_off_v = 0.0;
  I_sense_off_A = 0.0;
  long t_stop = micros() + itime_off_msec * 1000;
  while (micros() < t_stop) {
    float v_off_raw = ads.readADC_Differential_0_1() * ADC_V_per_ADU + V_RM_off_v;
    float i_off_raw = ads.readADC_Differential_2_3() * ADC_V_per_ADU_2 / R_sense;
    V_RM_off_v += v_off_raw;
    I_sense_off_A += i_off_raw;
    icounter_off++;
  }
  V_RM_thevenin_v = V_RM_off_v / icounter_off;
}
void func_meas_on() {
  long t_stop = micros() + itime_on_msec * 1000;
  icounter_on = 0;
  V_RM_on_v = 0.0;
  I_sense_on_A = 0.0;
  while (micros() < t_stop) {
    float v_on_raw = ads.readADC_Differential_0_1() * ADC_V_per_ADU + V_RM_on_v;
    float i_on_raw = ads.readADC_Differential_2_3() * ADC_V_per_ADU_2 / R_sense;
    V_RM_on_v += v_on_raw;
    I_sense_on_A += i_on_raw;
    icounter_on++;
  }
  V_loaded_v = V_RM_on_v / icounter_on;
  I_load_A = I_sense_on_A / icounter_on;
}

```